

## A 100W FIXED BIAS ULTRA-LINEAR AMPLIFIER

The circuit of this amplifier is given in Fig. 8 and it provides 100W output at 5% distortion with an h.t. potential of 560V. The performance is shown graphically in Fig. 9 and Table III gives the operating conditions for the output stage.

With fixed bias, the large change in anode current necessitates a low impedance power supply and, with normal rectifier circuits, an inductance-input-smoothing filter is essential. The smoothing capacitor should be of high value to prevent an instantaneous fall in h.t. potential upon the occurrence of a transient signal. Satisfactory performance will be obtained with a single inductor and a capacitance of 50–150 $\mu$ F. The circuit diagram shows two 160 $\mu$ F 450V electrolytic capacitors in series as an economical method of obtaining the required capacitance.

Reducing the h.t. potential to 460V, the load impedance to 4k $\Omega$  and the grid bias to -65V results in an amplifier giving 65W output. The performance of this version is shown in Fig. 10 and the appropriate operating data are included in Table III.

### Protection Against Bias Failure

Should the bias supply fail, the KT88 anode currents would increase excessively and it is recommended that some device be incorporated for protecting the output tubes in the event of bias failure. The arrangement illustrated in Fig. 11 inserts a suitable resistor into the output stage cathode circuit which will enable the amplifier to function temporarily at half maximum output.

A triode, which could be one half of a double triode used also in the first stage of the amplifier, is connected in series with a relay across the main h.t. supply. The relay contacts are normally closed and short-circuit the emergency cathode resistor R1. The triode is held at cut-off by the connection of its grid to the bias supply at a point about 50V negative to earth. Should the bias fail, the grid of the triode will rise to earth potential and current will flow through the triode. This energises the relay, the contacts of which will open and bring into circuit the cathode bias resistor.

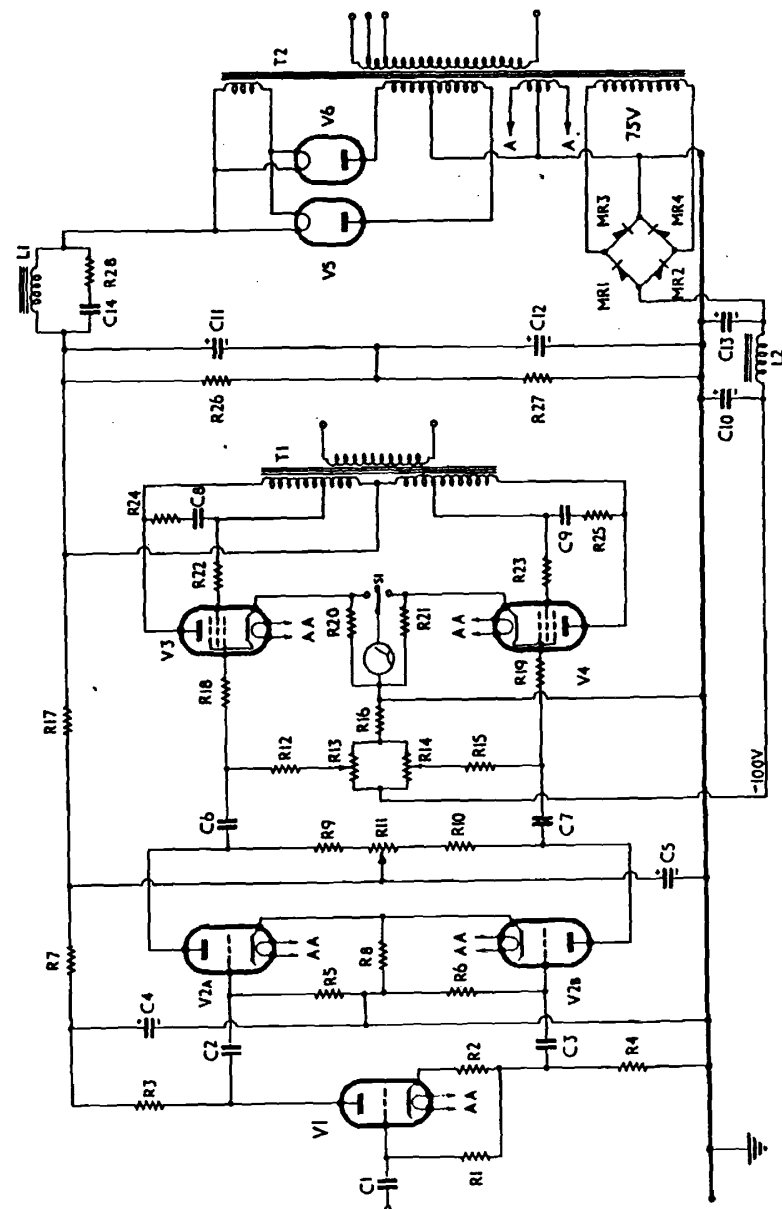


Fig. 8. Circuit diagram of the KT88 100W fixed bias ultra-linear amplifier. R26 and R27 equalise the voltages across C11 and C12, the series-connected smoothing capacitors. C14 and R28 prevent the build-up of high voltage transients across L1.

### COMPONENT VALUES FOR FIG. 8

#### 100W FIXED BIAS AMPLIFIER

##### GEC TUBES

- V1 L63/6J5
- V2 B65/6SN7
- V3 KT88
- V4 KT88
- V5) U19 (or GXU50 using separate HT transformer with delay)
- V6)

##### RESISTORS

(20%, 0.25W unless otherwise shown)

- R1 1M $\Omega$
- R2 1.5k $\Omega$
- R3 33k $\Omega$  1W
- R4 33k $\Omega$  1W) matched to 5%
- R5 470k $\Omega$  10%
- R6 470k $\Omega$  10%
- R7 33k $\Omega$  1W
- R8 1k $\Omega$
- R9 33k $\Omega$  10% 1W
- R10 33k $\Omega$  10% 1W
- R11 10k $\Omega$  (Pot)
- R12 68k $\Omega$  10% 0.5W
- R13 20k $\Omega$  w.w. preset
- R14 20k $\Omega$  w.w. preset
- R15 68k $\Omega$  10% 0.5W
- R16 10k $\Omega$  10% 1W
- R17 4.7k $\Omega$  1W
- R18 5.6k $\Omega$
- R19 5.6k $\Omega$
- R20) Meter shunts
- R21)
- R22 270 $\Omega$  0.5W
- R23 270 $\Omega$  0.5W
- R24 470-1500 $\Omega$  0.5W
- R25 470-1500 $\Omega$  0.5W
- R26 100k $\Omega$  10% 1W
- R27 100k $\Omega$  10% 1W
- R28 10k $\Omega$  0.5W

##### CAPACITORS

- C1 0.01 $\mu$ F
- C2 0.05 $\mu$ F
- C3 0.05 $\mu$ F
- C4 8 $\mu$ F 350V
- C5 8 $\mu$ F 450V
- C6 0.1 $\mu$ F
- C7 0.1 $\mu$ F
- C8 1000pF
- C9 1000pF
- C10 8 $\mu$ F 250V
- C11 160 $\mu$ F 450V) each 100+60
- C12 160 $\mu$ F 450V) dual
- C13 8 $\mu$ F 250V
- C14 0.01 $\mu$ F 750V

##### MISCELLANEOUS

- L1 5H 325mA
  - L2 20H 10mA
  - T1 100W Ultra-linear transformer  
4.5k $\Omega$  anode-anode (100W)  
4k $\Omega$  anode-anode (65W)  
Primary inductance: < 40H
  - Leakage inductances:  
Prim.-sec.: > 6mH  
½ prim.-UL tap: > 6mH
  - T2 Mains transformer  
Secondaries:  
\*650-0-650V to give  
325mA d.c.  
6.3V 5A CT  
4V 7A  
75V 10mA (bias)
  - S1 1-pole 3-way
  - MR1)
  - MR2)
  - MR3) 75V 10mA
  - MR4)
- \*If using GXU50, a separate H.T. transformer is required.

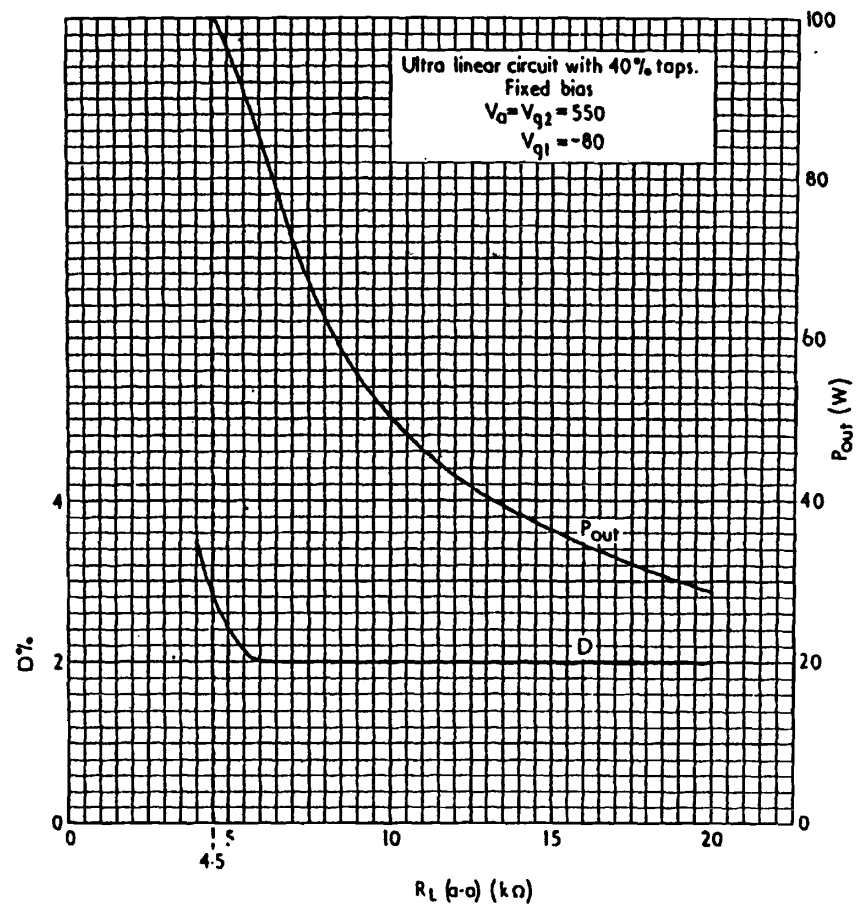


Fig. 9. Performance of the KT88 100W amplifier of Fig. 8.